

Section 2

Lab Quiz #1

ECE 242: Electronic Circuits 2 (Fall 2016)

Instructor: Bosco Leung

Name:

Student ID:

Lab Session (circle one): Tuesday Wednesday Thursday

Problem 1

Circuit A and circuit B are set up as shown in Figure 1. By changing the value of the variable resistor, R_L , I_o vs V_o graph for circuit A is generated as shown in Figure 2(a) and I_o vs V_o graph for circuit B is generated as shown in Figure 2(b). The data points for figure 2 are recorded as shown in Table 1.

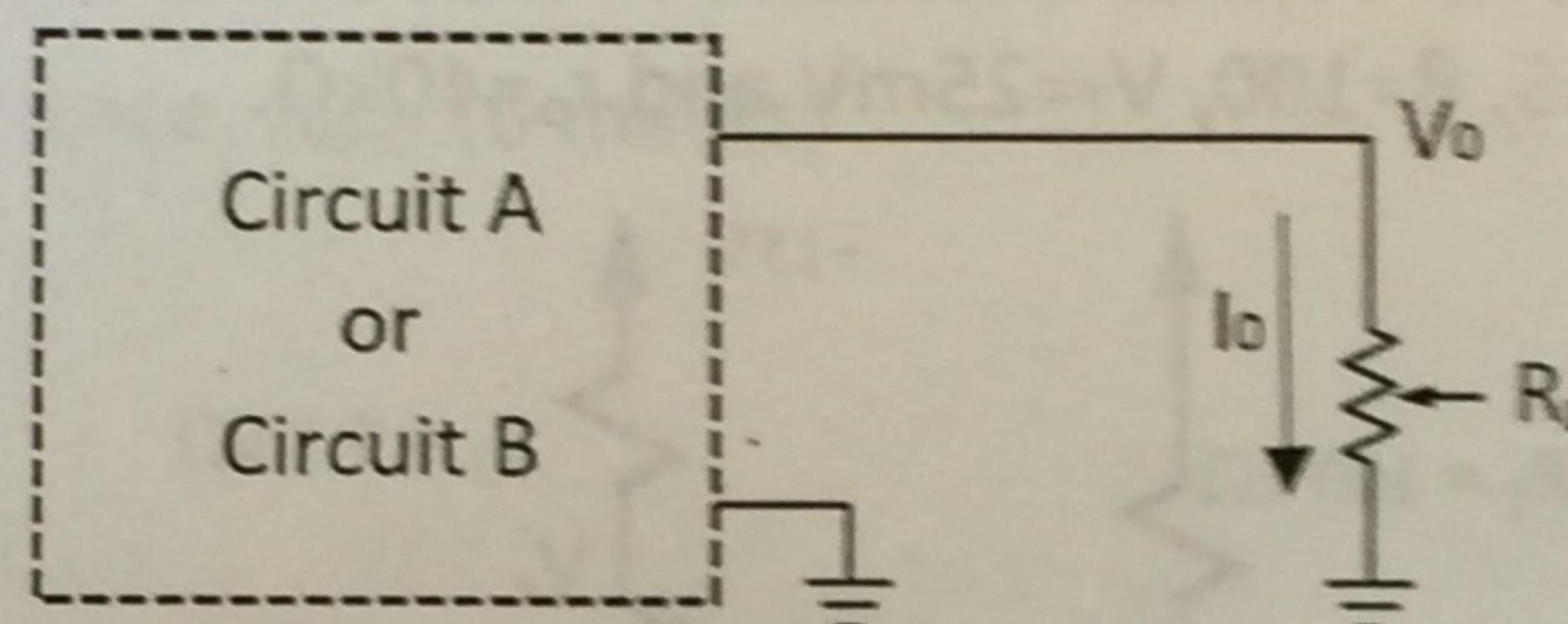


Figure 1: Laboratory Setup

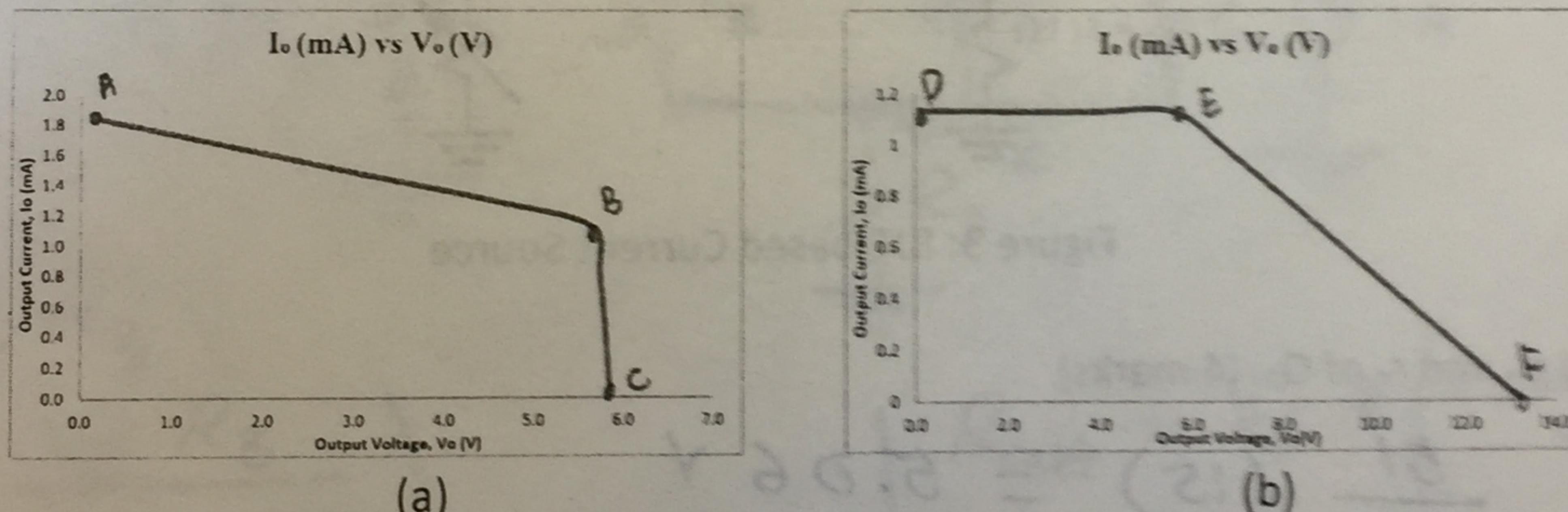


Figure 2: (a) I_o vs V_o graph of circuit A. (b) I_o vs V_o graph of circuit B


| Data Points | A | B | C | D | E | F |
|-------------|-------|------|--------|-------|------|-------|
| I_o (mA) | 1.83 | 1.19 | 0.0058 | 1.20 | 1.13 | 0.008 |
| V_o (V) | 0.025 | 5.70 | 5.86 | 0.022 | 5.85 | 13.4 |

Table 1: Data Points

- a) Which circuit is a better current source? Justify your answer. (2 marks)

Circuit "B". Circuit "B" has higher output resistance

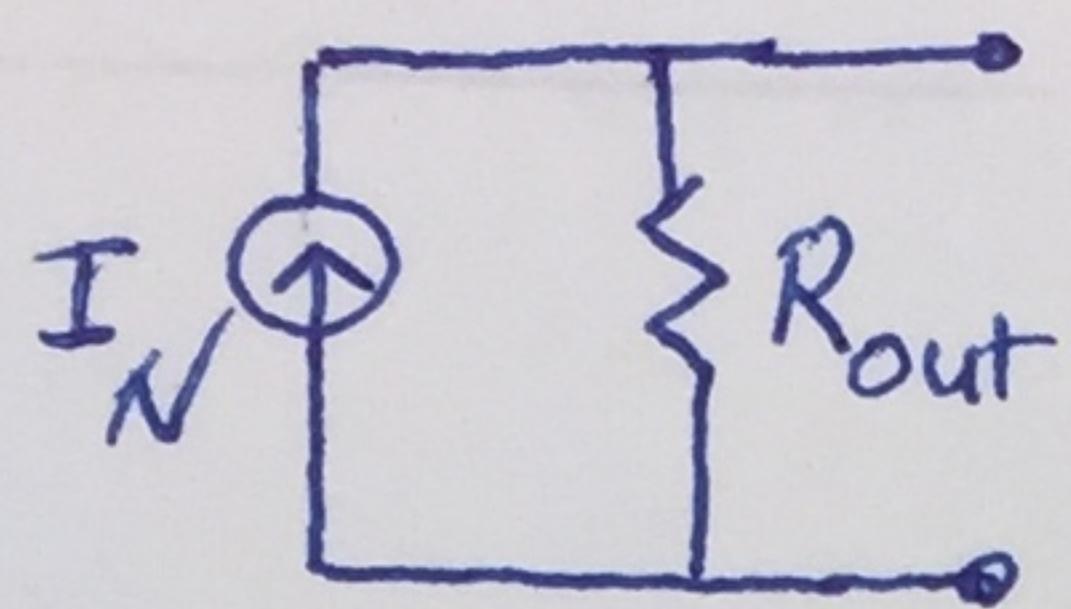- b) Draw a Norton or Thevenin (whichever appropriate) equivalent model for the circuit chosen in part (a). Label all components. (3 marks)



$$I_N = 1.13 \text{ A}$$

$$R_{out} = 6.73 \text{ k}\Omega$$

Problem 2

In Figure 3, the variable resistor, R_L is set to a value such that the BJT, Q_1 operates in forward active region. It is given that $|V_{be}|=0.65$, $\beta=100$, $V_T=25\text{mV}$ and $r_o=40\text{k}\Omega$.

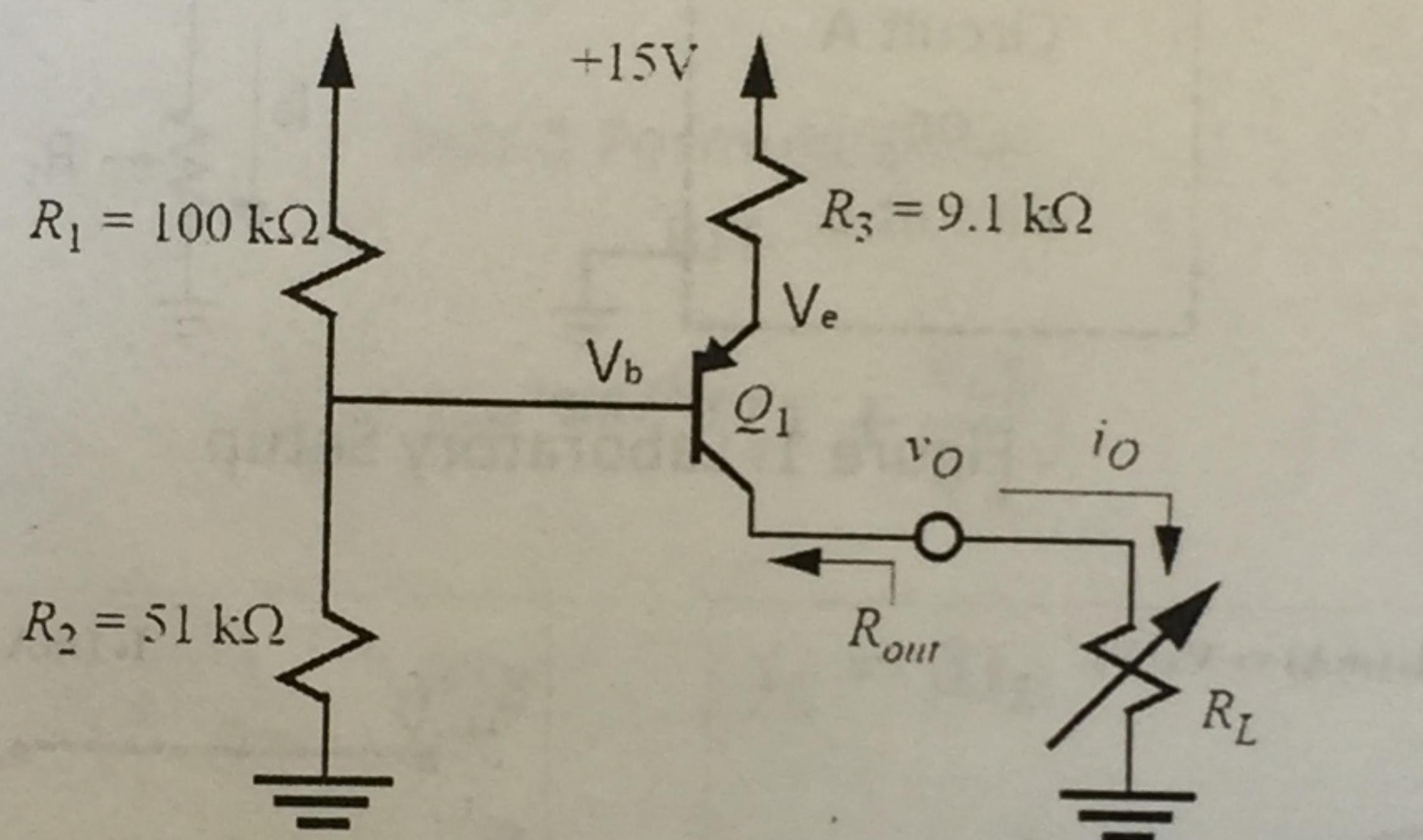


Figure 3: BJT-based Current Source

- (a) Find g_m and r_π of Q_1 . (4 marks)

$$V_b = \frac{51}{51+100} (15) = 5.06 \text{ V}$$

$$V_e = 5.06 + 0.065 = 5.12 \text{ V}$$


$$I_E = \frac{15 - V_e}{R_3} = \frac{15 - 5.12}{9.1k} = 1.02 \text{ mA}$$

$$I_C = \frac{100}{101} (1.02) = 1.010 \text{ mA}$$


$$\therefore g_m = \frac{1.010}{25 \text{ m}} = 0.0404 \text{ A/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.0404} = 2.475 \text{ k}\Omega$$

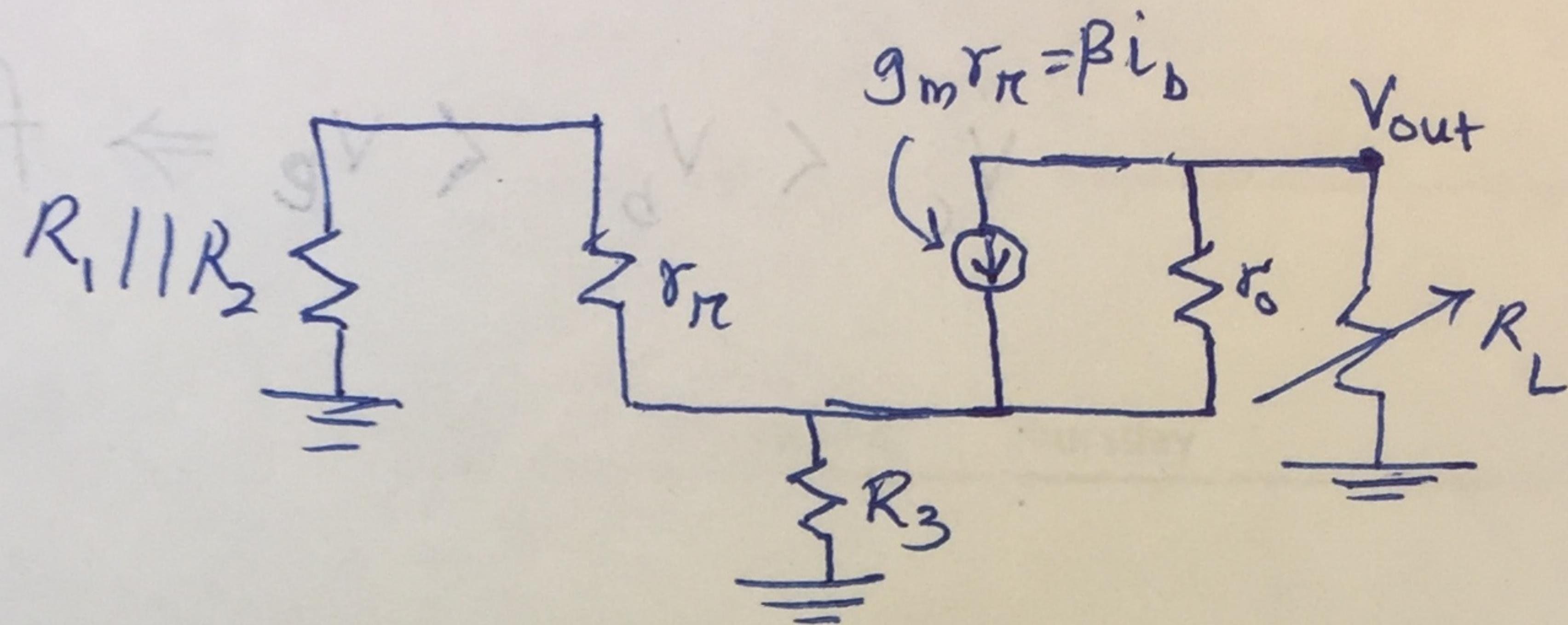(b) Draw the small signal model for the circuit in Figure 3. Label all components. (3 marks)



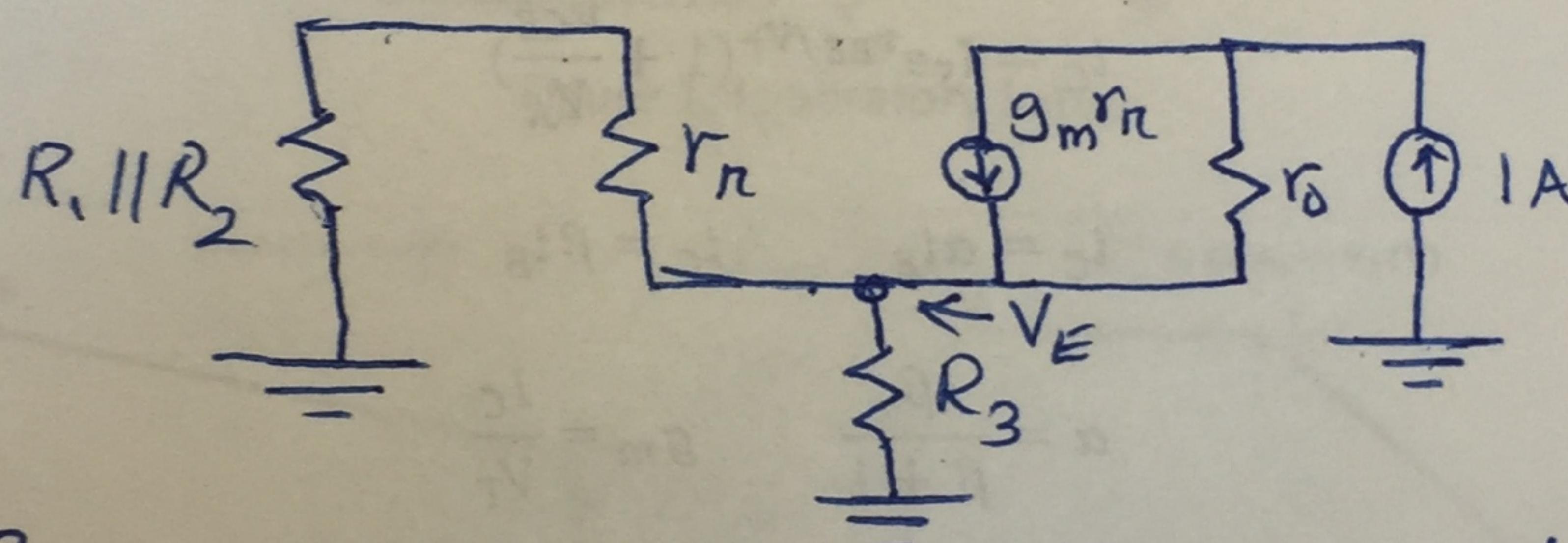c) Find the output resistance, R_{out} . (6 marks)



$$V_E = (1 - i_b) R_3$$

$$= \left(R_3 - \frac{V_E R_3}{r_N + R_1 \parallel R_2} \right)$$

$$V_E \left(1 + \frac{R_3}{r_N + R_1 \parallel R_2} \right) = R_3$$

$$\therefore V_E = \frac{R_3}{1 + \left(\frac{R_3}{r_N + R_1 \parallel R_2} \right)}$$

$$V_E = \frac{9.1k}{1 + \left(\frac{9.1k}{2.475k + 100k/15k} \right)}$$


$$V_E = 7.274 kV$$

$$\begin{aligned} R_{out} &= V_E + (1 - g_m V_N) r_o \\ &= V_E + \left(1 + g_m \frac{V_E r_N}{r_N + R_1 \parallel R_2} \right) r_o \\ &= r_o + \left(1 + \frac{g_m r_N r_o}{r_N + R_1 \parallel R_2} \right) V_E \\ R_{out} &= 40k + \left(1 + \frac{(100)(40k)}{2.475k + 100k/15k} \right) * (7.274k) \end{aligned}$$

$$\therefore R_{out} = 1.055 M\Omega$$

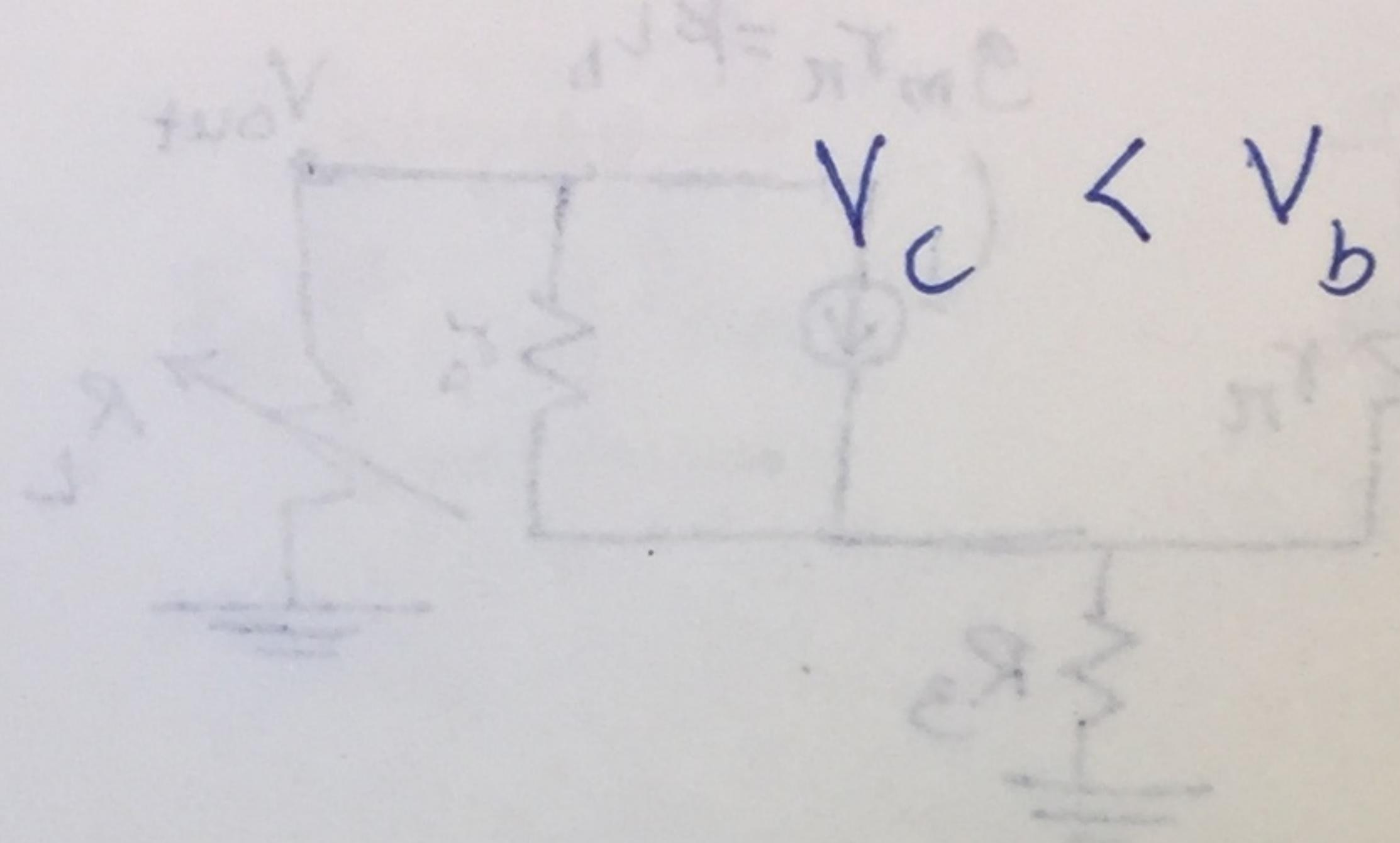d) What is the region of operation for BJT, Q₁ when R_L is set to 3kΩ. Justify your answer. (2 marks)

When $R_L = 3\text{k}\Omega$; $V_o = 1.010 \times 3\text{k} = 3.03\text{ V}$



$V_C < V_b < V_E \rightarrow$ forward active

Quiz 1 Formula Sheet

BJT

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A}\right)$$

$$i_C = \alpha i_E \quad i_C = \beta i_B$$

$$\alpha = \frac{\beta}{\beta + 1} \quad g_m = \frac{I_C}{V_T}$$

$$\delta(V_{AC} - 1) + \beta V = r_0 = \frac{V_A}{I_C}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{\beta}{g_m} = (\beta + 1)r_e$$

$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$

$$\frac{(V_{AC})(001)}{R_L(300) + 300r_e + 1} + 2104 = 200$$

$$(21F5.5)*$$

$$2M 220.1 = 200$$

$$\left(\frac{20}{300,000 + 300r_e + 1}\right) + 1$$

$$\left(\frac{20}{300,000 + 300r_e + 1}\right) + 1$$